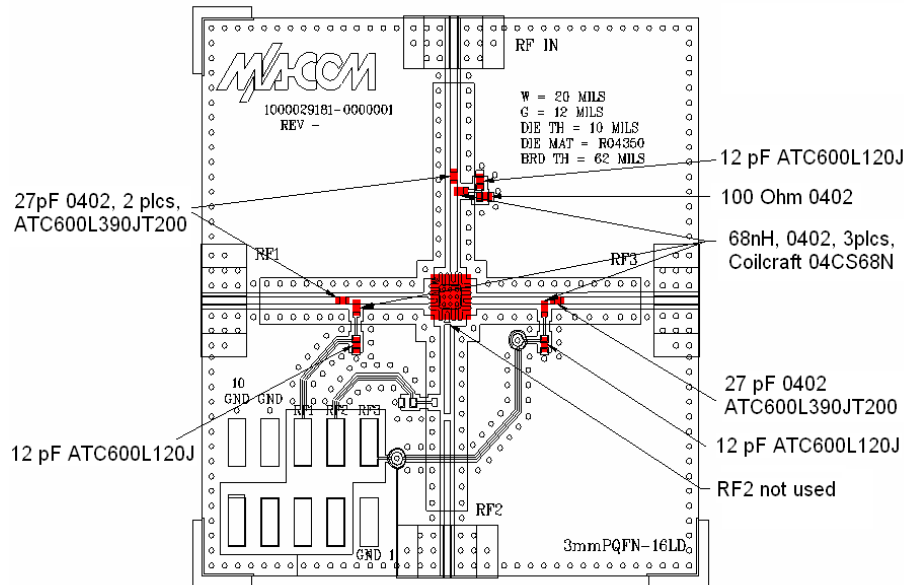


Figure 3. Sample board layout



The board was specifically designed for the new series of high power switches and therefore is interchangeable. The component selection and RF ports are specific to part number and operating frequency. In figure 3. the component selection is specific to the MASW-000822-12770T switch and as shown in the drawing the RF2 is cut and not used.

In this case the board is intended to be biased with a negative & positive supply. The schematic in Figure 4. shows the schematic representation of the board and switch. The intention of this board was use the TX and RF ports for the bias paths, however , the device can be biased as any SPDT switch.


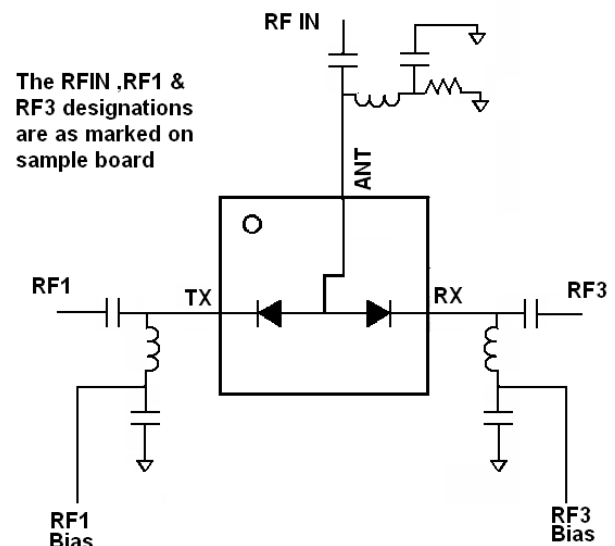


Figure 4. Sample Board Schematic

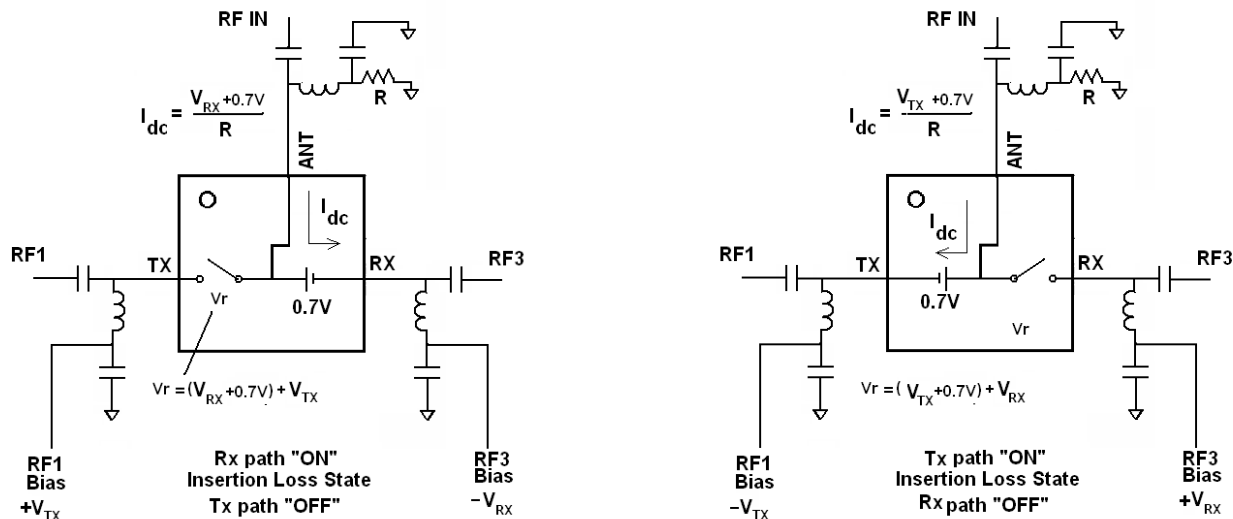


DC Current	Rx-Antenna RF Condition	Tx-Antenna RF Condition
$I_{DC} = -10 \text{ or } -20 \text{ mA}$ $V_r(T_X), +40 \geq 0V$	Low Loss	Isolation
$I_{DC} = -10 \text{ or } -20 \text{ mA}$ $V_r(R_X), +40 \geq 0V$	Isolation	Low Loss
$V_{DC}, +40 \geq 0V$ $V_r(T_X) \& V_r(R_X), +40 \geq 0V$	Isolation	Isolation

Figure 5. Dual Positive and Negative Supply Biasing

As mentioned, the sample board supplied accommodates only when there are dual polarity supplies available. The schematic representation shows the biasing required to turn the PIN diodes "ON" and "OFF" for signal transmission and isolation. The truth table shows the reverse bias voltage through the device and current draw for Low Loss and Isolation states of Tx and Rx arms.

In order to accommodate biasing when a single positive supply is available, it is required that bias be available

through the Antenna port. This can be achieved with slight modification of the existing sample board. The 100 ohm resistor would be removed and a "jumper" wire would have to be soldered at the point where the shunt capacitor and bias choke intersect. The schematic representation Figure 6. shows the use of a single positive supply to achieve same results. In order to achieve proper isolation in the "OFF" arm, the back bias (V_r) on the devices should be large enough to sustain higher power levels.

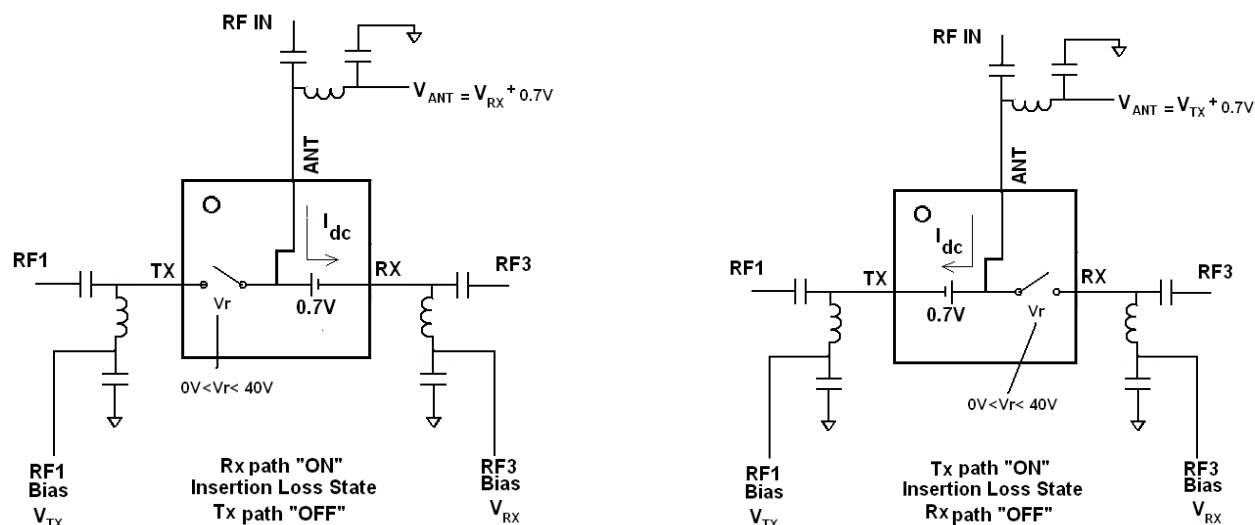

DC Current	Rx-Antenna RF Condition	Tx-Antenna RF Condition
$I_{DC} = -10$ or -20 mA $V_{r(TX)}, +40 \geq 0V$	Low Loss	Isolation
$I_{DC} = -10$ or -20 mA $V_r (RX), +40 \geq 0V$	Isolation	Low Loss
$V_{DC}, +40 \geq 0V$ $V_{r(TX)} \& V_{r(RX)}, +40 \geq 0V$	Isolation	Isolation

Figure 6. Single Positive Supply Biasing